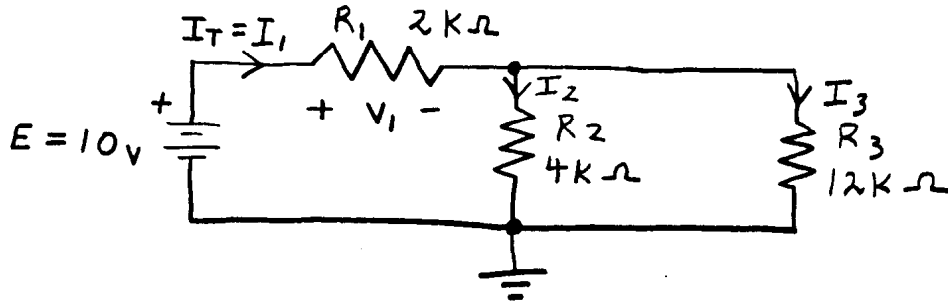


C. SMITH  
EET / 23  
OCT. 33, 1999

5-4 GIVEN THE FOLLOWING CKT:



(a) FIND THE TOTAL CURRENT  $I_T$ .

$$R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(4 \times 10^3)(12 \times 10^3)}{4 \times 10^3 + 12 \times 10^3} = \frac{48 \times 10^6}{16 \times 10^3} = 3 \times 10^3 \Omega$$

$$R_T = R_1 + R_2 \parallel R_3 = 2 \times 10^3 + 3 \times 10^3 = 5 \times 10^3 \Omega$$

$$I_T = \frac{E}{R_T} = \frac{10V}{5 \times 10^3 \Omega} = 2 \times 10^{-3} A = \boxed{2 \text{ mA}}$$

(b) FIND THE VOLTAGE ACROSS  $R_1$ .

$$V_1 = I_T \times R_1 = (2 \times 10^{-3}) (2 \times 10^3) = \boxed{4 \text{ V}}$$

5-5 FOR PROBLEM 5-4 FIND THE FOLLOWING:

(a)  $I_2$ .

$$I_2 = \frac{R_3}{R_2 + R_3} \times I_T = \frac{12 \times 10^3}{4 \times 10^3 + 12 \times 10^3} \times 2 \times 10^{-3}$$

$$= \frac{12 \times 10^3}{16 \times 10^3} \times 2 \times 10^{-3} = 1.5 \times 10^{-3} A = \boxed{1.5 \text{ mA}}$$

(b)  $I_3$ .

$$I_3 = I_T - I_2 = 2 \text{ mA} - 1.5 \text{ mA} = \boxed{0.5 \text{ mA}}$$