

PURDUE UNIVERSITY NORTH CENTRAL

Electrical & Computer Engineering Technology Department

ECET 157 (Prof. Smith)

TEST #2

Spring, 2009

NAME: ANSWERS

Part I - Sinusoidal Waveforms.


(15 points)

1. For the signal below, determine the following. $V_{dc} = \underline{0V}$ $V_{ampl} = \underline{10V}$
 $V_{rms} = \underline{7.07V}$ $V_{pk} = \underline{10V}$ $V_{p-p} = \underline{20V}$ $V_{ave} = \underline{0V}$

$f = \underline{50K}$ Hz period = $\underline{20\mu s}$ phase shift = $\underline{+90^\circ}$ $\omega = \underline{314K}$ rad/s

Write the time domain equation for the signal. $v(t) = \underline{10 \sin(314Kt - 90^\circ)}$

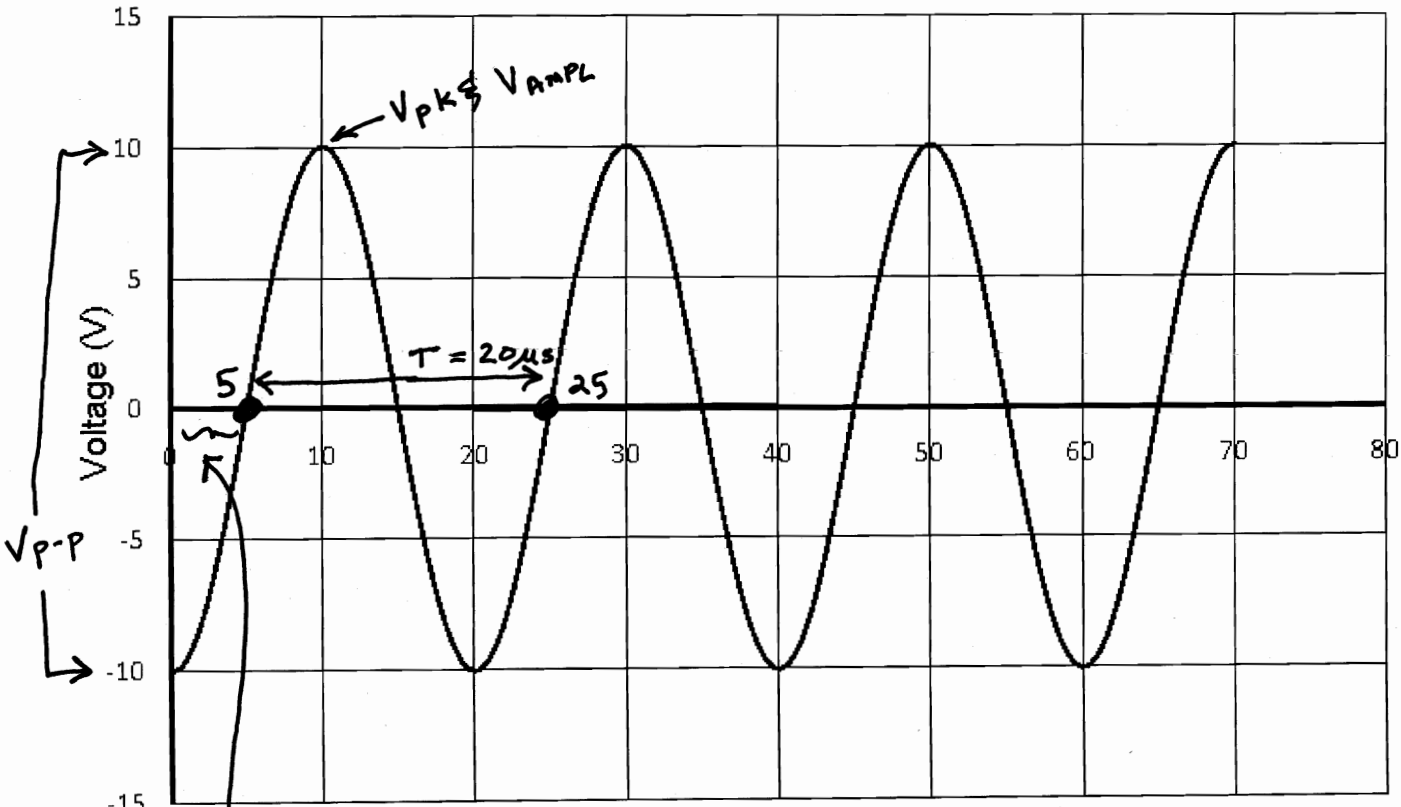Write the phasor notation for the signal. $\bar{V} = \underline{7.07V \angle +90^\circ}$



Time shift = $+5\mu s$

$$\theta = \frac{\text{Time shift}}{T} \times 360^\circ = \frac{+5\mu s}{20\mu s} \times 360^\circ = +90^\circ$$

2 * π * 50K = 314K

Part II - - True-False and Write-In Questions.

(30 points)


2. T F The p-side of a diode is called the anode.
3. T F A BJT in saturation typically has 0.2 Volts or less across the collector-emitter ~~junction~~ ^{connection.}
4. T F As a semiconductor gets warmer, it conducts more current.
5. T F A Zener diode ~~used~~ can be driven to the reverse breakdown point, then recover.
6. The three terminals of a bipolar junction transistor are called:
 a. Collector
 b. Base
 c. Emitter
8. The Q-point indicates the (name the current) I_C current and the (name the voltage) V_{CE} voltage when the transistor's input is equal to (how many?) 0 Volts.
9. The three notable features that make op amps so useful are: (Also tell why each is important.)
 a. Hi Z_{in} \rightarrow Draws almost zero current from previous ckt.
 b. Low Z_{out} \rightarrow Sends most power to load.
 c. Large Gain \rightarrow Useful amplifier.
10. Looking at a schematic, you notice that the input v_{in} to an op amp circuit goes to the (-) input terminal through a resistor. You also notice that there is a feedback resistor connected from the output to the same (-) terminal. What type of amplifier is this? (Check best answer.)
 ___ a. Non-Inverting Amplifier. b. Inverting Amplifier. ___ c. Voltage Follower.
11. Briefly describe how an op amp's Input Offset Voltage (V_{IO}) and Input Bias Current (I_B) can affect the circuit. (Is this something to be concerned about? If so, why?)
ADDS VOLTAGE TO OUTPUT, SO V_{out} WILL HAVE AN ERROR.
ERROR MAY BE AMPLIFIED BY SUBSEQUENT AMPLIFIERS AND EVEN SEND OUTPUT TO EDGE.

Part III -- BJT Amplifier Circuit.

(25 points)

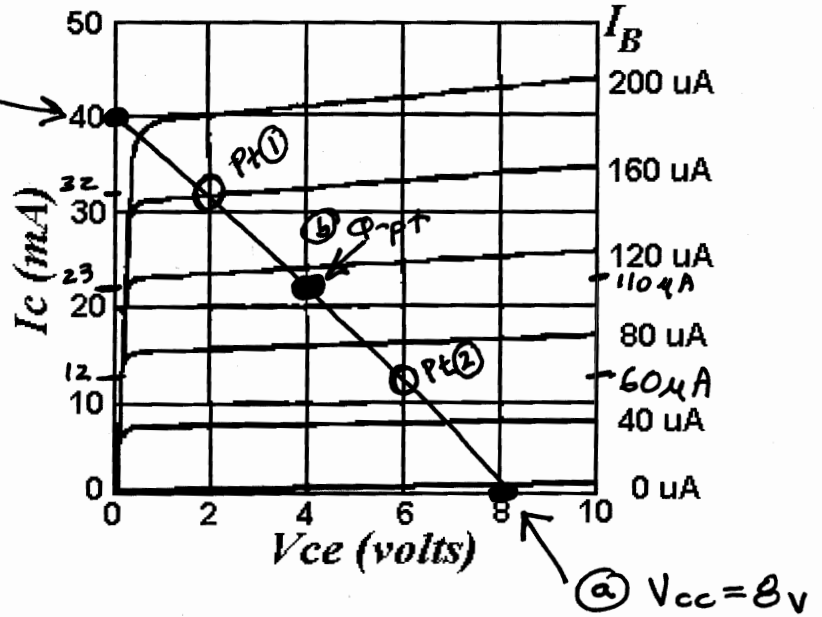
12. Refer to the characteristic curve shown.

- ✓ (a) Use $V_{CC} = 8V$ and $I_{C(max)} = 40 mA$ and label these on the plot.
- ✓ (b) Pick a Q-point & label it. (Clearly mark its I_C & V_{CE} !!!)
- ✓ (c) Calculate the β .
- ✓ (d) Calculate the α .
- ✓ (e) Draw the universal-bias circuit.
- (f) Calculate R_a , R_b , R_c and R_e and label these values on your circuit. (Use the approximate method.)
- (g) Calculate I_B , I_C and I_E .
- (h) Calculate the AC gain.



(c) $\beta = \frac{I_C}{I_B} \approx \frac{23mA}{110\mu A} = \boxed{209}$

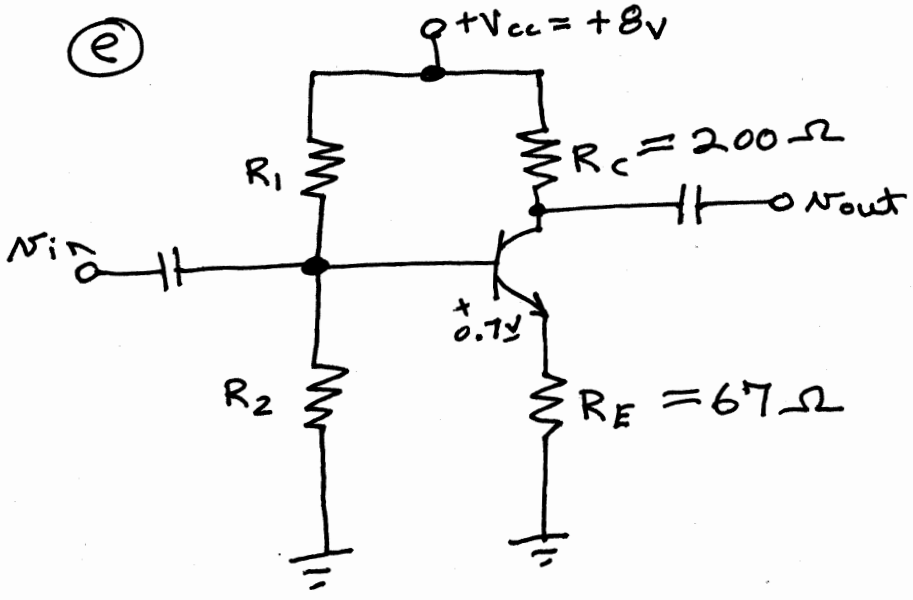(d) $\alpha = \frac{\beta}{\beta + 1} = \frac{209}{210} = \boxed{0.995}$



$$\textcircled{f} R_c \cong \frac{V_{cc}}{I_{c_{max}}} = \frac{8V}{40mA} = \boxed{200\Omega}$$

Pg. 35

$$R_E \cong \frac{1}{3} R_c = \boxed{67\Omega}$$

CALCULATE I_C & I_E , THEN V_E & V_B (Part g.)

$$\text{From (g)} I_E \cong 23mA \Rightarrow V_E = R_E I_E = 67\Omega \times 23mA = 1.54V$$

$$\Rightarrow V_B = V_E + 0.7V = 1.54 + 0.7 = 2.24V$$

$$\text{choose } R_1 + R_2 = 80K\Omega \Rightarrow R_2 = \boxed{22.4K\Omega}$$

I.E. EACH 1V
NEEDS 10K Ω .

$$R_1 = 80K - R_2$$

$$= 80K - 22.4K$$

$$= \boxed{57.6K\Omega}$$

\textcircled{g} READ FROM CHAR. CURVE:

$$\text{At Q-point, } \boxed{I_C \cong 23mA} \text{ \& \ } \boxed{I_B \cong 110\mu A}$$

$$\boxed{I_E} = I_C + I_B = \boxed{23.110mA}$$

$$\cong I_C \cong 23mA$$

\textcircled{h} AC Gain: Pick 2 points, one above and one below the Q-pt. (labelled Pt ① and Pt ②.)

$$\Delta I_C = I_{C1} - I_{C2} = 32mA - 12mA$$

$$= 20mA$$

$$\Delta I_B = I_{B1} - I_{B2} = 160\mu A - 60\mu A$$


$$= 100\mu A$$

$$\beta_{AC} = \frac{\Delta I_C}{\Delta I_B} = \frac{20mA}{100\mu A} = \boxed{200}$$

Part III -- BJT Amplifier Circuit.


(30 points)

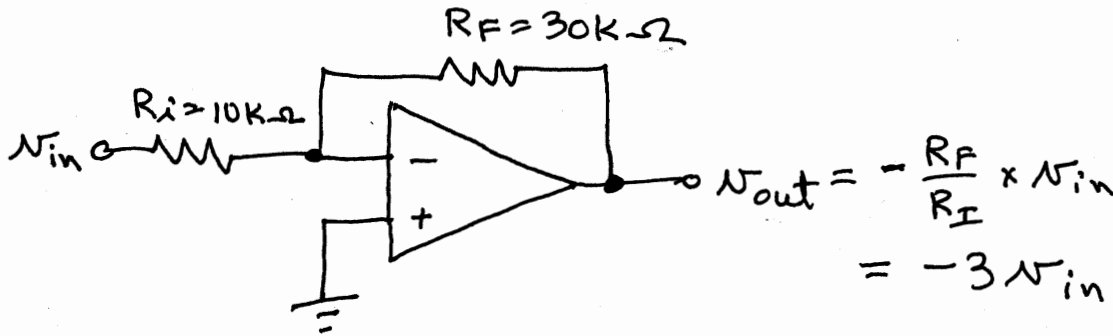13. Draw an Inverting Amplifier Circuit with a gain of 3. $GAIN = -\frac{R_F}{R_I} \Rightarrow$ USE $R_I = 10K\Omega$
 $R_F = 30K\Omega$



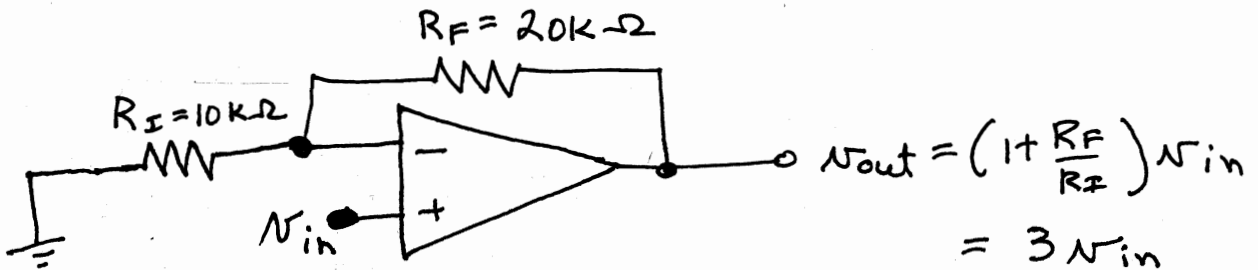14. Draw a Non-Inverting Amplifier Circuit with a gain of 3.

$GAIN = 1 + \frac{R_F}{R_I} = 3 \Rightarrow \frac{R_F}{R_I} = 2 \Rightarrow$ USE $R_I = 10K\Omega$
 $R_F = 20K\Omega$



15. Draw a Voltage Follower Circuit.

