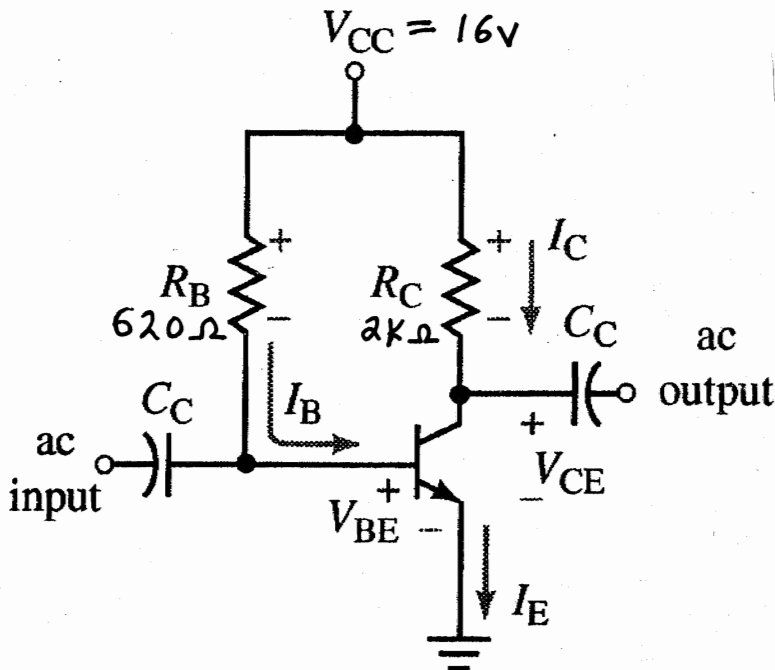



21) $\beta = 120 \leftarrow \frac{I_c}{I_B}$

ANSWERS
CH 28: 21, 31, 43 & 45.



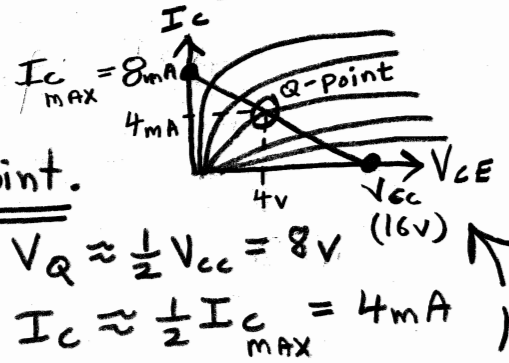a) "Saturation" means
 • I_c is at max.
 • $V_{CE} \approx 0V$.

Since $V_{CE} = 0$,
 $V_{R_c} = V_{CC} = 16V$
 So, $I_{c_{SAT}} = \frac{V_{R_c}}{R_c} = \frac{16V}{2k\Omega}$
 $= 8mA$



b) Find I_B, I_c, I_E and V_{CE} at Q-point.

Q-point is located in middle $\Rightarrow V_Q \approx \frac{1}{2} V_{CC} = 8V$
 $\Rightarrow I_c \approx \frac{1}{2} I_{c_{MAX}} = 4mA$

So, $V_{CE} = 4V$ and $I_c = 4mA$.

$I_B = \frac{I_c}{\beta} = \frac{4mA}{120} = 33\mu A$

$I_E = I_c + I_B = 4mA + 33\mu A = 4.033mA$

c) See load line here

31) $\beta = 120$


a) "Saturation" means that $V_{CE} \approx 0$.

$\Rightarrow V_{CC} (16V)$ drops across $R_C + R_E$

$$\Rightarrow I_{C_{SAT}} = \frac{V_{CC}}{R_C + R_E} = \frac{16V}{1.5K + 510}$$

$$= 7.96mA$$

$$\approx 8mA$$

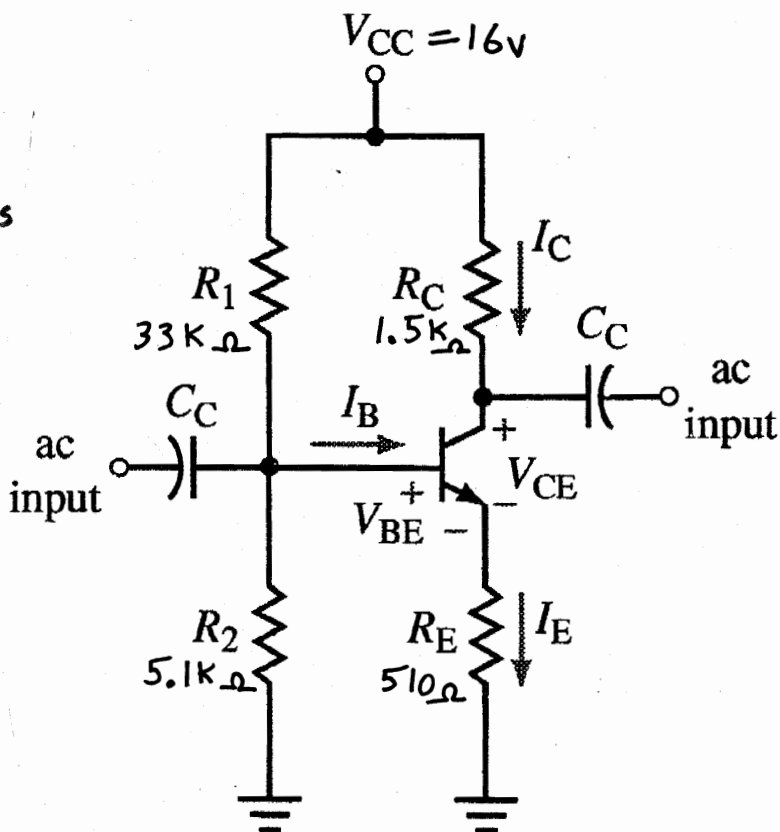

b) Solve for I_B, I_C, I_E & V_{CE} at Q-point.

Endpoints of load line are $I_{C_{MAX}} = I_{C_{SAT}} = 8mA$

and $V_{CE} = V_{CC} = 16V$


Q-point is in middle $\Rightarrow V_{Q_{pt}}^{CE} = \frac{1}{2} V_{CC} = 8V$

$I_{Q_{pt}}^C = \frac{1}{2} I_{C_{MAX}} = 4mA$

$$I_B = \frac{I_C}{\beta} = \frac{4mA}{120} = 33\mu A$$

$$I_E = I_C + I_B = 4mA + 33\mu A = 4.033mA$$

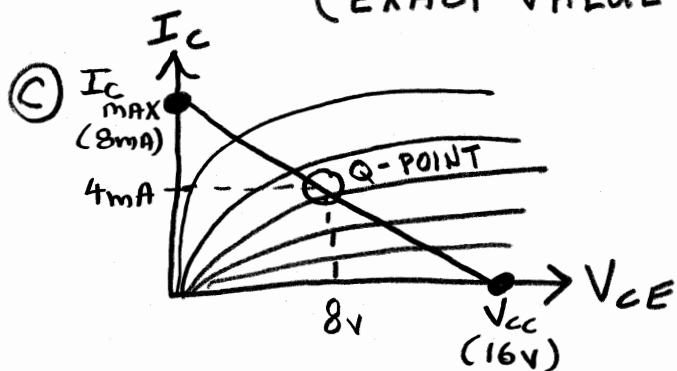(EXACT VALUE = $3.98mA + 33\mu A = 4.013mA$)



(43) NOTE: Problem says $R_C = 470\Omega$,
 but diagram says 430Ω .
 I will use the 470 Ω value.


(a) $I_{C\text{ SAT}} = I_{C\text{ MAX}}$

Remember that
 "saturation"
 means $V_{CE} = 0$.

$\Rightarrow V_{CC}$ drops across
 only R_C and
 the LED.

$\Rightarrow V_{R_C} = V_{CC} - V_{LED}$
 $= 8V - 1.6V$
 $= 6.4V$

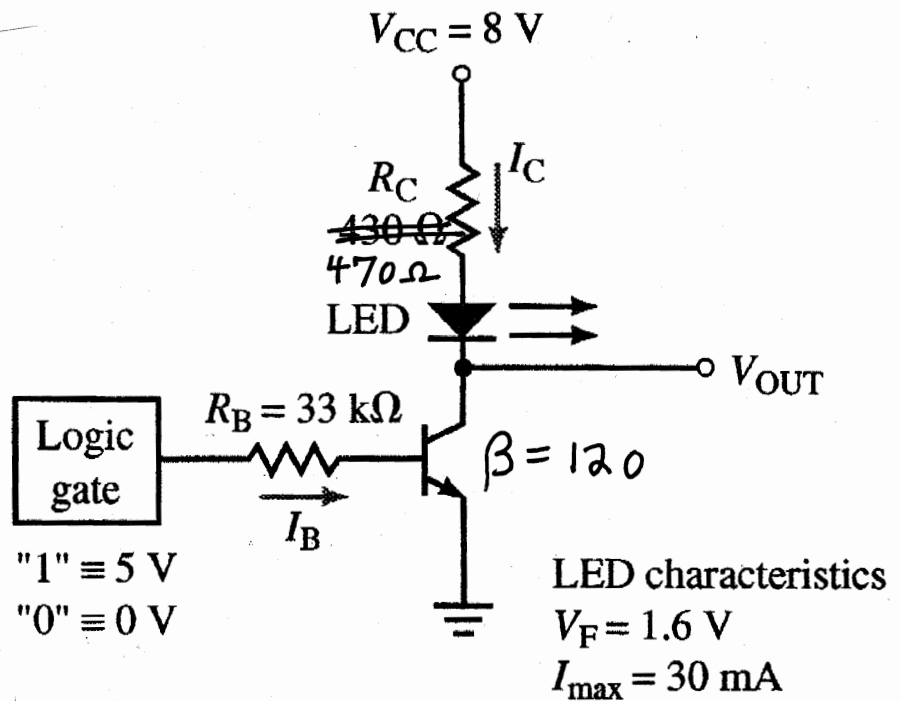$\Rightarrow I_C = \frac{6.4V}{470\Omega}$
 $= \boxed{13.6\text{ mA}}$



(b) If Logic gate is Logic 1 \Rightarrow Transistor is ON.
 \Rightarrow Transistor saturated.

$V_{R_C} = 8V - V_F$
 $= 8V - 1.6V = 6.4V$

$I_C = \frac{V_{R_C}}{R_C} = \frac{6.4V}{470\Omega} = \boxed{13.6\text{ mA}}$

$\Rightarrow V_{CE} = 0$

(c) In Part (a), transistor is saturated. $\Rightarrow V_C = V_{CE} = \boxed{0V}$

(d) Logic gate at Logic 0 \Rightarrow Transistor is OFF.

$\Rightarrow I_C = 0 \Rightarrow I_{LED} = \boxed{0A}$

(e) In (d) $I_C = 0 \Rightarrow V_{OUT}$ floats to $V_{CC} = \boxed{+8V}$


④⑤ Pin 1 (+) Pin 2 (-) $\Rightarrow 0.223K\Omega \Rightarrow$ Conducts.
 Pin 2 (+) Pin 1 (-) $\Rightarrow \infty \Omega \Rightarrow$ No conduction.

Pin 2 (+) Pin 3 (-) $\Rightarrow \infty \Omega \Rightarrow$ No conduction.
 Pin 3 (+) Pin 2 (-) $\Rightarrow 0.259K\Omega \Rightarrow$ Conducts.


Pin 1 (+) Pin 3 (-) $\Rightarrow \infty \Omega$
 Pin 3 (+) Pin 1 (-) $\Rightarrow \infty \Omega$ } MUST BE
 OUTER PINS
 \Rightarrow C and E

Step 1: Pins that give ∞ both ways are
 the outer (C and E) connections.
 \Rightarrow Know that 2 must be the Base.

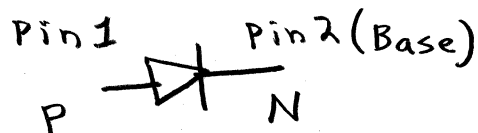Step 2: Pin 1 (+) Pin 2 (-) conducts.
 \Rightarrow Pin 1 must be P-type
 and Pin 2 must be N-type.



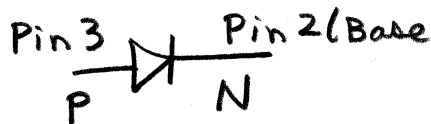Step 3: Pin 3 (+) Pin 2 (-) conducts.
 \Rightarrow Similar to Pins 1 & 2.



② Thus Pin 3 - Pin 2 - Pin 1 are P-N-P.

③ Pin 2 is Base. Pins 1 & 3 are C & E, but do
not know which is which!