

Answers - ECET 157  
Ch. 30: 9, 12, 13, 16 & 20.

Inverting Amplifier:  $N_{out} = -\frac{R_F}{R_i} \times N_{in}$

$$= -\frac{100K}{20K} \times (-2.0V)$$

$$= \boxed{-10.0V}$$

⑫ Same ckt as ⑨, except  $R_i = 7.5K\Omega$  and gain = -4.

$$\text{Gain} = -\frac{R_F}{R_i} = -4$$

$$\Rightarrow -\frac{R_F}{7.5K\Omega} = -4$$

$$\Rightarrow R_F = 4 \times 7.5K\Omega = \boxed{30K\Omega}$$

⑬ Non-Inverting Amplifier  $\Rightarrow \text{Gain} = 1 + \frac{R_F}{R_i}$

$$R_F = 100K\Omega, R_i = 20K\Omega$$

a)  $\text{Gain} = 1 + \frac{R_F}{R_i} = 1 + \frac{100K}{20K} = 1 + 5 = \boxed{6}$

b) Input goes straight into non-inverting input.

$$\Rightarrow \boxed{R_{in} = 2M\Omega}$$

c)  $R_{out} = 75\Omega \parallel (R_F + R_i) = 75\Omega \parallel 120K\Omega$


$\nearrow$   
Op Amp's  
 $Z_{out}$

$\approx 75\Omega$  since  
 $R_F \ll R_i$  are  
so big.

d) For  $N_{in} = -2.0V$ ,  $N_{out} = \left(1 + \frac{R_F}{R_i}\right) N_{in} =$

$$= \left(1 + \frac{100K}{20K}\right) (-2.0V) = \boxed{-12V}$$

⑩ Want non-inverting ckt with gain = 4.

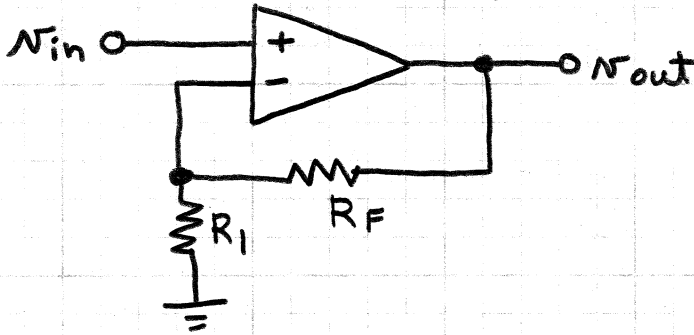

$$\text{Gain} = 4 = 1 + \frac{R_F}{R_1} \Rightarrow \frac{R_F}{R_1} = 3$$

$$\Rightarrow R_F = 3 \times R_1$$

Pick any pair of resistors that satisfy this equation.

E.g.,  $R_F = 90\text{K}\Omega$  and  $R_1 = 30\text{K}\Omega$ .

⑪ Normally,  $V_{out} = V_{in}$  for voltage follower ckt.

But with  $V_{io} = 2\text{mV}$

$$V_{out} = V_{in} \pm 2\text{mV}$$

NOTE: This is important.  
The offset may be (+) or (-). You don't know which unless you measure it!